

# EE537 Circuit Simulation Lab

## Experiment 8

Name: <PRIKSHAT SHARMA>

ID Number: <2023EEM1023>

November 7, 2023

AIM: Design of an inverting amplifier using a two stage OTA.

### 1 Design of an inverting amplifier using a two stage OTA

 


Figure 1: Inverting amplifier with capacitive voltage feedback

Spec.	Value
Midband gain	20 dB
Bandwidth	> 1 MHz
Input capacitance	1 pF
Load capacitance	10 pF
Slew rate	$\geq 10 \text{ V}/\mu\text{s}$
Gain error	0.1 %
Phase margin	$\geq 65^\circ$
Operating temperature range	0 °C to 70 °C

Figure 2: Given Specifications

**1.1 Implement the 2 stage using a miller compensated 2 stage OTA. Show the calculations used for all the specifications and detailed design procedure.**

#### 1.2 Mathematical analysis

##### 1.2.1 Finding poles without miller compensation

The Circuit is as above but without the  $C_c$ . Considering the pole between stage 1 and 2 as  $P_1$ . The pole is given by

$$P_1 = \frac{-1}{(r_{onm0} || r_{opm3})C_{o1}} \quad (1)$$

Here  $C_{o1}$  is the internal parasitic capacitances between stage 1 and 2.  $P_2$  is the pole considered for stage 2 i.e. the point from where the output is taken.

$$P_2 = \frac{-1}{C_l(r_{onm3} || r_{opm1})} \quad (2)$$

Here the capacitance taken is the output capacitance only. The minus sign represents the Left half Poles.

 


Figure 3: Ckt for calculations of Open loop gain and phase margin

### 1.2.2 Finding zero without miller Capacitor

The zero considered here is between the pmos PM1 and PM3. The impedance seen from the gate of PM1 is

$$\text{impedance} = \frac{1}{g_{pm1}} \parallel r_{opm1}$$

$$Z = \frac{1}{\left(\frac{1}{g_{pm1}} \parallel r_{0pm1}\right) C_p} \quad (3)$$

The  $C_p$  here is the internal capacitance seen from the gate of pm1.

### 1.2.3 Transfer Function

The transfer function of the uncompensated OTA is given by:

$$L(s) = \frac{-A_o(1 - \frac{s}{Z})}{(1 + \frac{s}{P_1})(1 + \frac{s}{P_2})} \quad (4)$$

where  $A_o$  is the Dc gain of the circuit.

### 1.2.4 Finding Poles for Compensated OTA

In compensated opamp a capacitor is used to slow the response of the system and make it appear like a 1st order system with the gain of the higher order system and the stability of the 1st order system. Here the  $P_1$  and  $P_2$  are on the same positions as for the case of uncompensated opamp.

$$w_{P1} = \frac{1}{g_{pm2} C_c (r_{nmo} \parallel r_{pm3}) (r_{pm2} \parallel r_{nm3})} \quad (5)$$

The above calculation is done using the Miller theorem because of which gain of the pm2 is used.

$$w_{P2} = \frac{gm_{Pm2}}{C_c + C_l} \quad (6)$$

which is equal to

$$\frac{gm_{pm2}}{C_l}$$

### 1.2.5 Finding Zeroes of the compensated Opamp

$$Z = \frac{gm_{pm2}}{C_c} \quad (7)$$

All other zeroes are neglected as they appear to be at very high frequencies and because of which their effect is minute on the response.

### 1.2.6 Loop Gain of compensated opamp

$$L(s) = \frac{A_o C_2}{(1 + \frac{s}{w_{P1}})(1 + \frac{s}{w_{P2}})(C_1 + C_2)} \quad (8)$$

$A_o$  is the dc gain

### 1.2.7 Finding relations between different parameters

$$\text{Slew rate} = 10V/\mu s$$

$$SR = \frac{Id_{through NM2}}{C_c} = \frac{I(NM3)}{C_c + C_l + \frac{C_1 C_2}{C_1 + C_2}} \quad (9)$$

as

$$\frac{C_1 C_2}{C_1 + C_2} \ll C_c + C_l$$

we can write

$$SR = \frac{I(NM3)}{C_c + C_l} \quad (10)$$

Phase margin of the circuit is given by

$$PM = 180 - \tan^{-1}\left(\frac{w_u}{w_{p1}}\right) - \tan^{-1}\left(\frac{w_u}{w_{p2}}\right) - \tan^{-1}\left(\frac{w_u}{w_z}\right) \quad (11)$$

Because we need the zero far away from the  $w_u$  that's why the last term goes to zero.  $w_{p1}$  is very small as compared to the  $w_u$ .

$$65 = 180 - 90 - \tan^{-1}\left(\frac{w_u}{w_{p2}}\right) \quad (12)$$

which gives

$$\frac{w_u}{w_{p2}} = \tan 25 \quad (13)$$

or  $w_{p2} = 2.14w_u$

$$w_z = 10w_u \quad (14)$$

### 1.2.8 Finding Unity gain bandwidth frequency

As  $A_f = 1$  is the limiting value so we can write, where  $f$  is the feedback factor,

$$\frac{A_o C_2}{(1 + \frac{s}{P_1})(C_1 + C_2)} = 1 \quad (15)$$

as  $jw$  is greater than 1 we can write

$$\frac{A_o P_1 C_2}{(C_1 + C_2)jw} = 1 \quad (16)$$

or

$$w = P_1(\text{LoopGain}) \quad (17)$$

or

$$w = \frac{g_{nm1}(r_{nm0}||r_{pm3})g_{PM2}(r_{nm3}||r_{pm2})C_2}{g_{pm2}C_c(r_{nm3}||r_{pm2})(r_{nm0}||r_{pm3})(C_1 + C_2)} \quad (18)$$

$$w_u = \frac{g_{nm1}C_2}{C_c(C_1 + C_2)} \quad (19)$$

Putting the values in the above equation relating  $w_z$  and  $w_u$  we get

$$\frac{g_{pm2}}{C_c} = \frac{10g_{nm1}C_2}{C_c(C_1 + C_2)} \quad (20)$$

or we get

$$g_{pm2} = g_{nm1} \quad (21)$$

Using the other equation

$$w_{P2} = 4w_u \quad (22)$$

we get

$$C_c = 0.4C_l \quad (23)$$

the feedback factor is

$$\frac{C_2}{C_1 + C_2} = 0.1 \quad (24)$$

Now using the slew rate equations (9) and (10)

$$I_{nm2} = 10^7(4)(10^{-12}) = 40\mu A \quad (25)$$

The equation 10 gives us

$$I_{NM3} = 10^7(10p + 4p) = 140\mu A \quad (26)$$

Now we have the currents so we can easily find the values of the aspect ratios For the current source below the differential amplifier we can say

$$40\mu = \frac{300\mu W(V_{GS} - V_T)^2}{2L} \quad (27)$$

Considering the overdrive voltage to be 0.1V. We get,

$$W/L = 80/3 \quad (28)$$

by intuition we can say that the nmos transistors of the differential amplifier is 40/3 Similarly we can argue that the pmos transistors present in the differential pair will have the W/L to be 80/3 because of the difference in the mobility values. Similarly we can solve for the W/L values of the Current source in the Second stage of the OTA.

$$140\mu = \frac{300\mu W(0.01)}{2L} \quad (29)$$

and we get the value to be equal to 280/3. Similar arguments as above are valid for the PMOS transistor of the 2nd stage of the OTA. Hence the W/L of Pmos is 560/3.

## 2 Show all the plots required to verify the achieved specifications.

 


Figure 4: Ckt for calculations of Open loop gain and phase margin

The gain of the OTA observed is around 77.97dB and the phase margin is  $180^\circ - 106.612^\circ = 73.388^\circ$

 


Figure 5: Plot of gain and phase margin

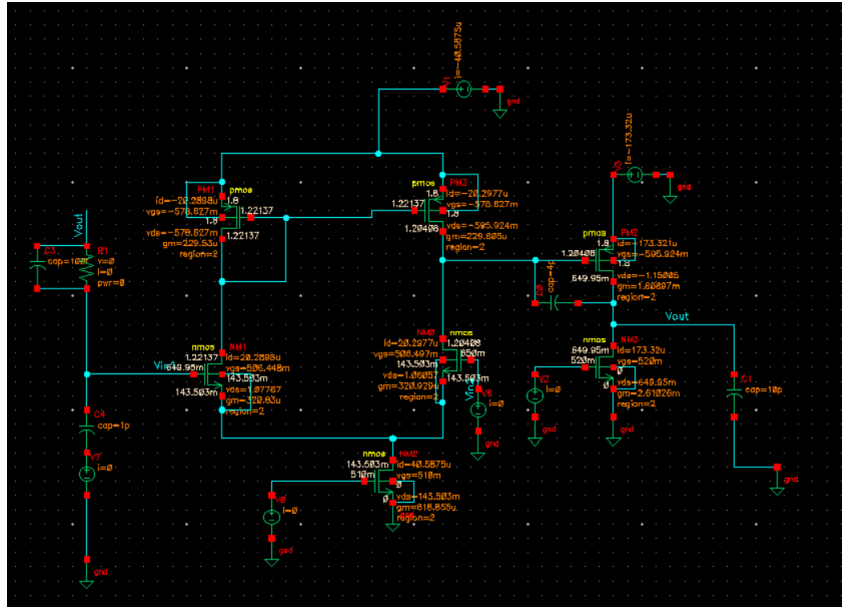


Figure 6: Extended Ckt diagram of Inverting amplifier

The closed gain of the inverting amplifier is 19.9987dB and the bandwidth is 1.01361MHz -1.6453Hz > 1MHz

$$Gain_{error} = \frac{A}{1 + Af} - \frac{1}{f} \quad (30)$$

$$\frac{\delta A}{A} = \frac{-1}{Af(1 + Af)} \approx 0.01266\text{percent} \quad (31)$$

 


Figure 7: Gain, bandwidth plot